



Introduction to Basic Electronics

Students please sign
in for the TW
Workshop!



<https://go.umd.edu/TWSP25>

Part 1




The Physics

What are Electronics?

Devices that **move electrons around** to accomplish something

- Remote control cars
- Phones
- Robots
- House lighting

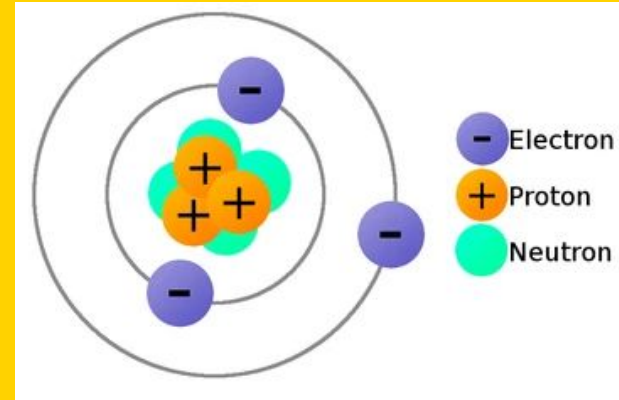
Electrons are tiny particles in matter that carry **built-in electric charge**.



Current

The speed with which electric charge moves

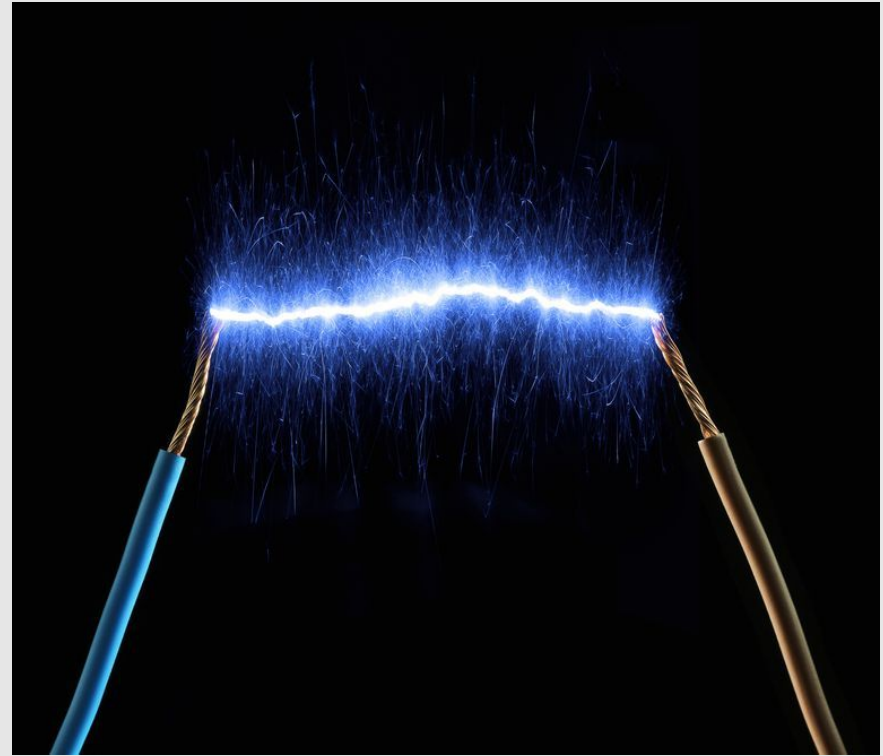- Formally, the amount of charge moving past a point per second
- Current is the **agent of change** in circuits; no current, no change!



Symbol: I

Unit: Ampere

Voltage

The energy used (or gained!) by moving charge from one point to another



$$V_{AB} = V_A - V_B$$


Symbol: V

Unit: Volt

- Charge is lazy, so current likes to **flow down voltage “drops”** from higher to lower voltage
- Voltage is a **relative potential energy** between two points
- We often assign a reference point that all voltages in a circuit are measured relative to. This is **ground**

Resistance

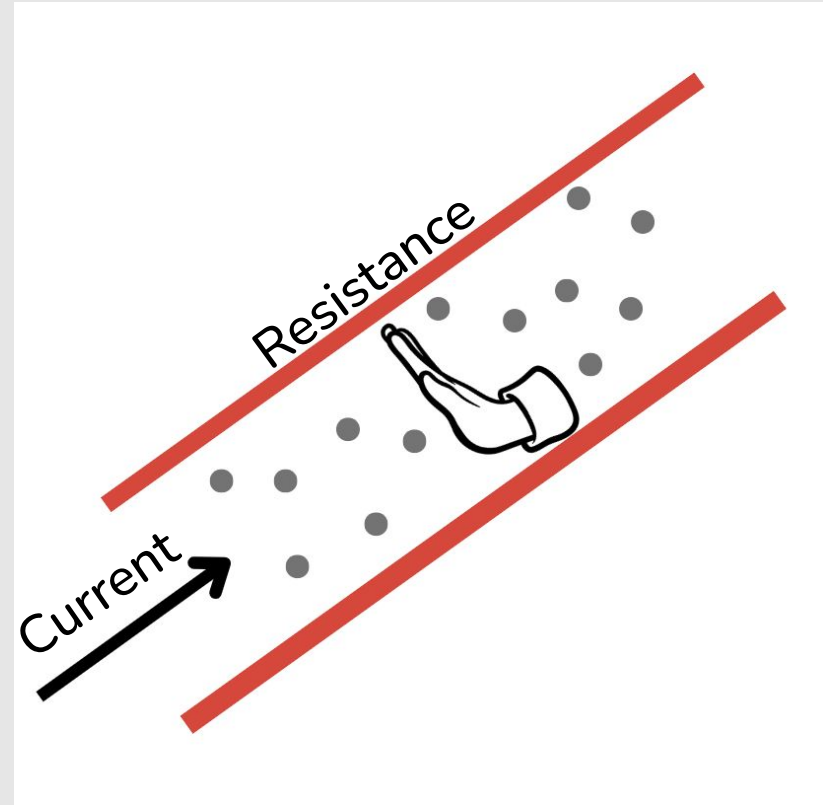- All materials steal kinetic energy from charge flowing through them and dispel it as heat - **resistance is the rate of theft**
- TLDR: resistance slows current flow!



Symbol: R


Unit: Ohms

Ohm's Law

Quantifies the relationship
between current, voltage, and
resistance


$$V = IR$$

Voltage = Current · Resistance

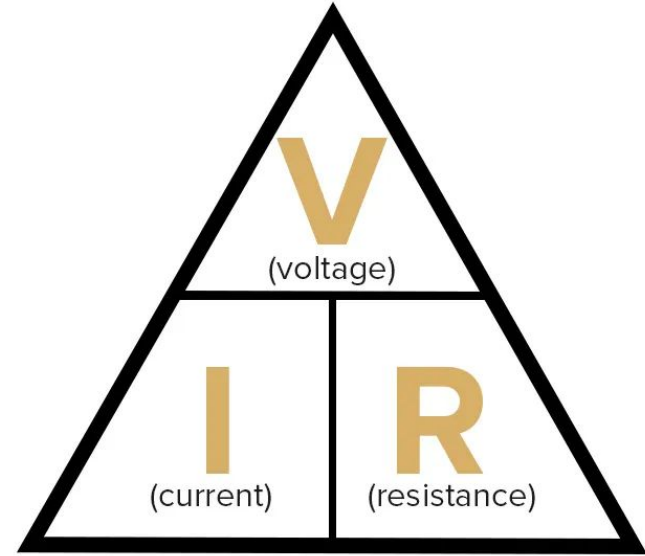

Devices which obey Ohm's law (eg. resistors, wires) are called **ohmic**!


The Hill Analogy

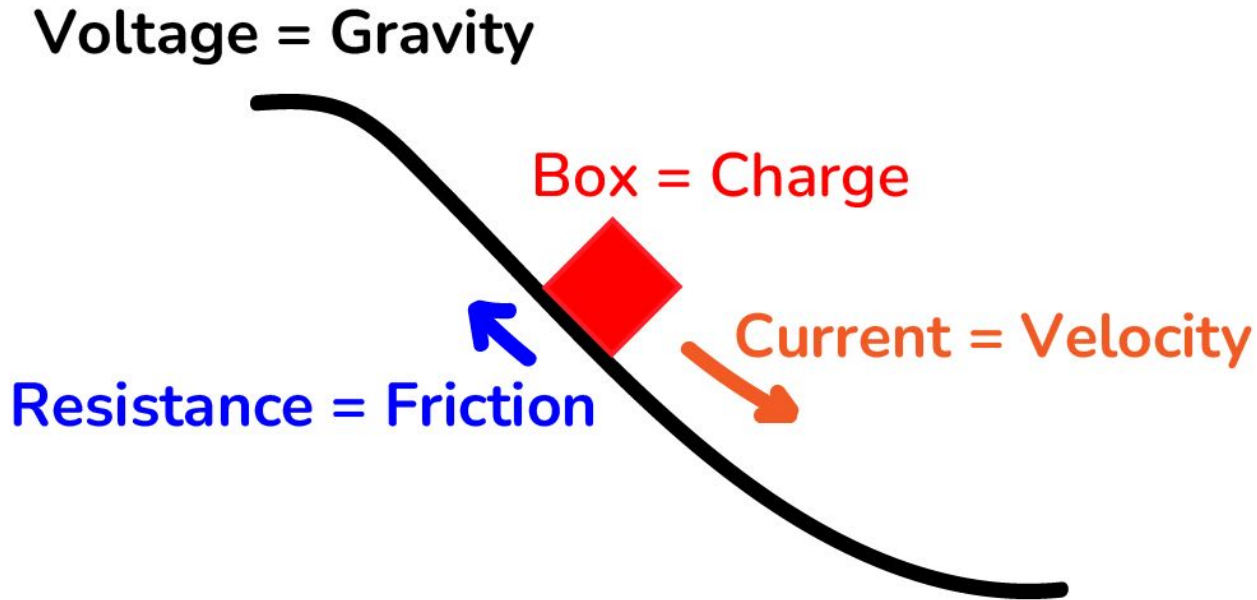

What is a Circuit?

Current only flows through closed loops called circuits.

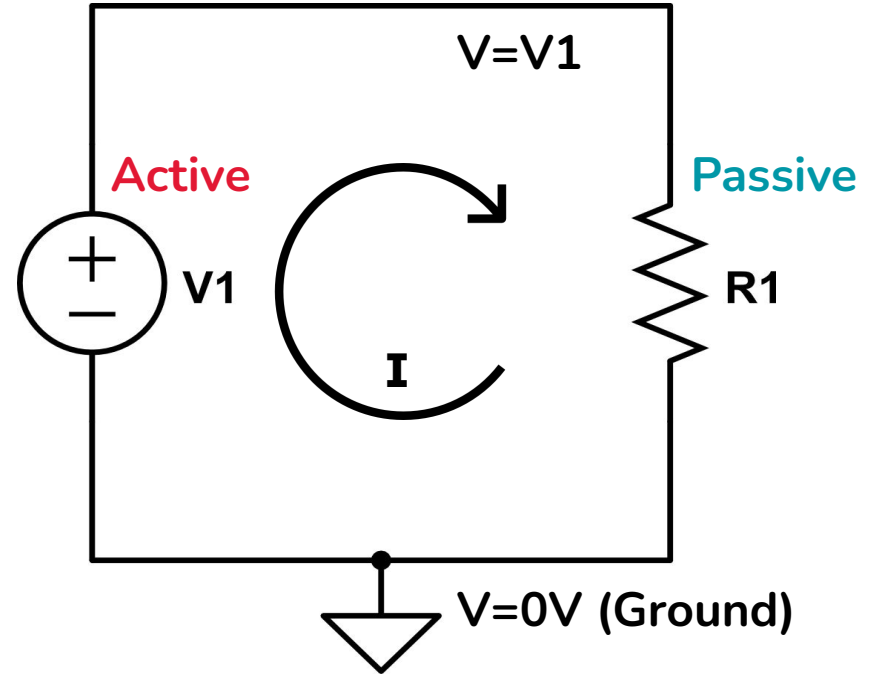- **Active** parts supply power, so current flows along voltage rises
- **Passive** parts consume power, so current flows along voltage drops



Power

- $\text{Power} = \text{Voltage} * \text{Current}$
- Energy used per second
- Measured in Watts
- Most components and devices have max power rating



Part 2



Basic Components

Power Supplies

- Sources of power
- Use an outlet connection to convert power to convert power
- Safe, reliable, and versatile




Batteries

- Store their own energy (measured typically in mWh) that is limited in quantity
- Can either be rechargeable (Li, NiCd, NiMH) or single use (alkaline)
- Portable
- Harder to use than benchtop power supplies (voltage varies across lifetime, limited current delivery/high ESR)



Basic Electronic Components

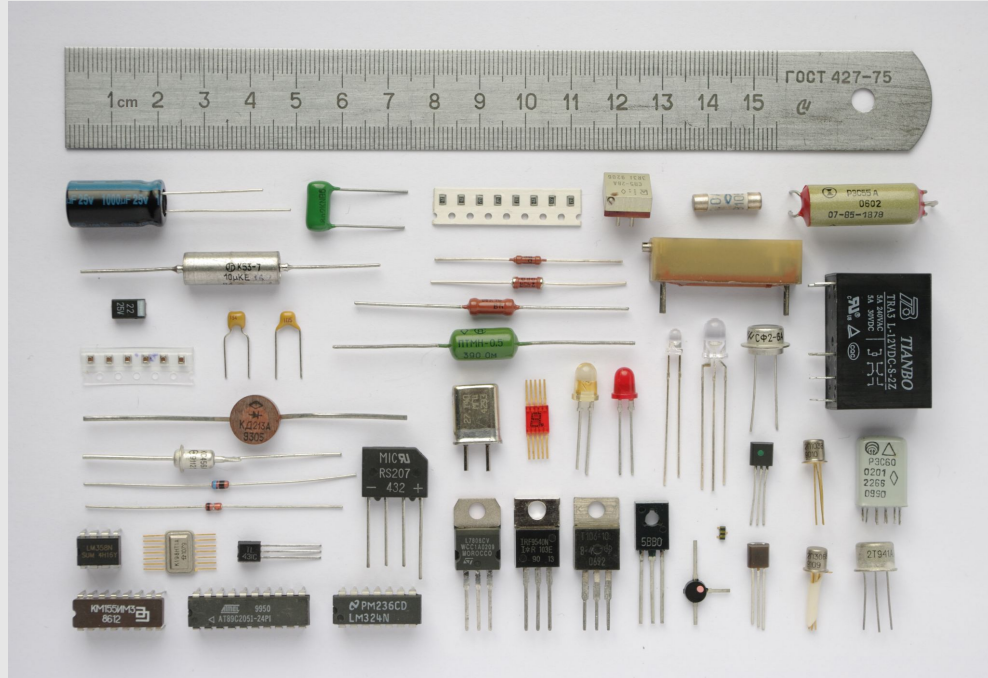


Resistors

- Component with designed resistance
- Follows Ohm's law
- $V=IR$
- Resists the flow of current



Capacitors


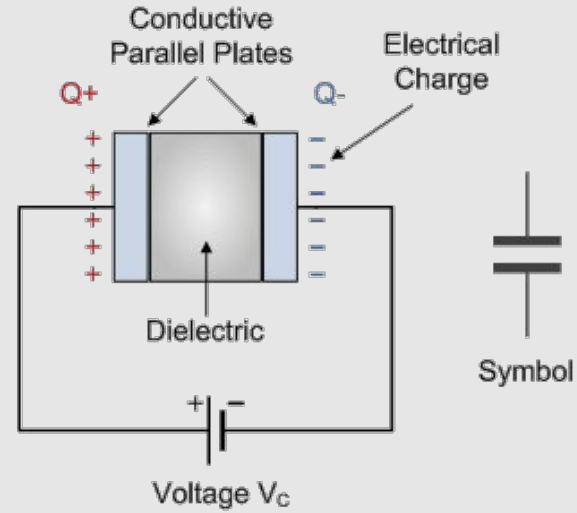
- Stores electric energy
- Metal plates separated by gap
- When voltage increases, charge accumulates on plates
- When voltage decreases, charge flows from plates



Inductors



- Stores magnetic energy
- Coil of wire
- Current causes a magnetic field around coil
- Opposes a change in current

Inductor Symbols

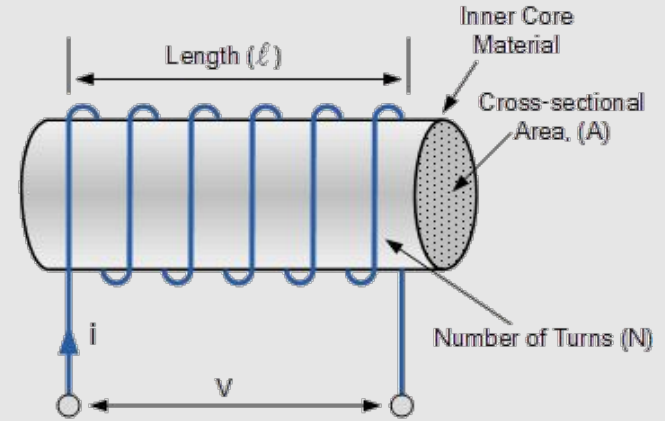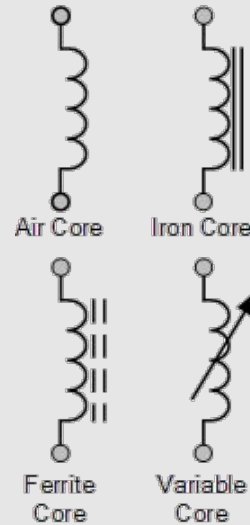


Diodes

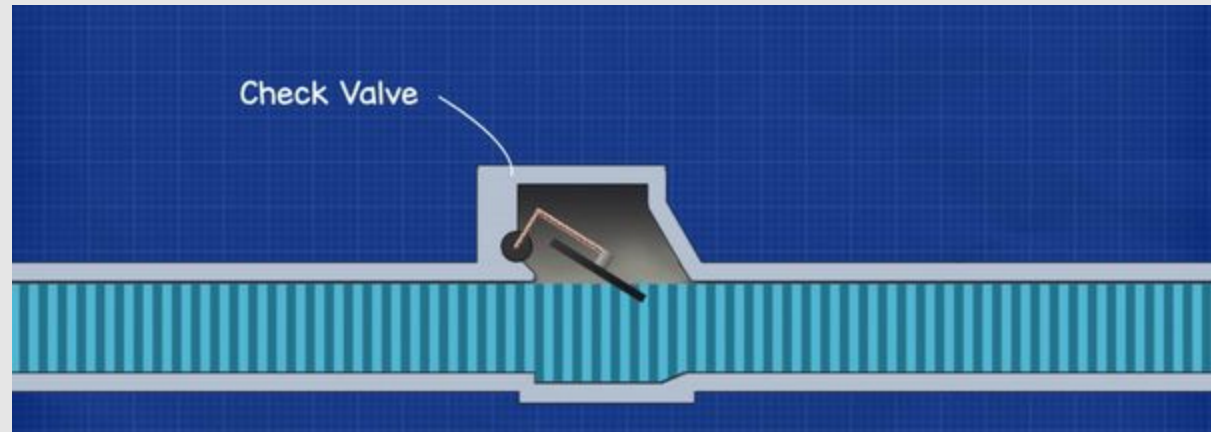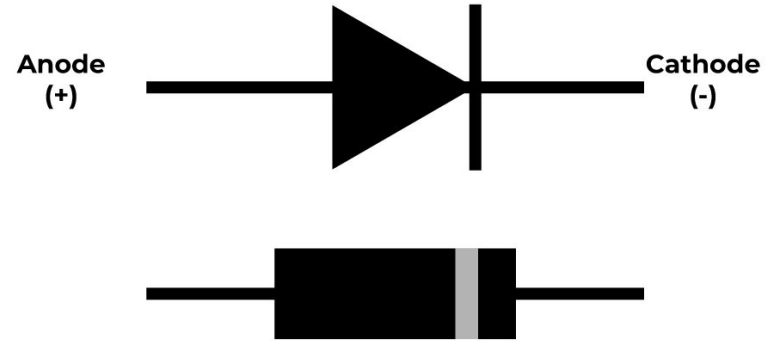- Allow current to flow in one direction
- Electrical check valves




Breadboard

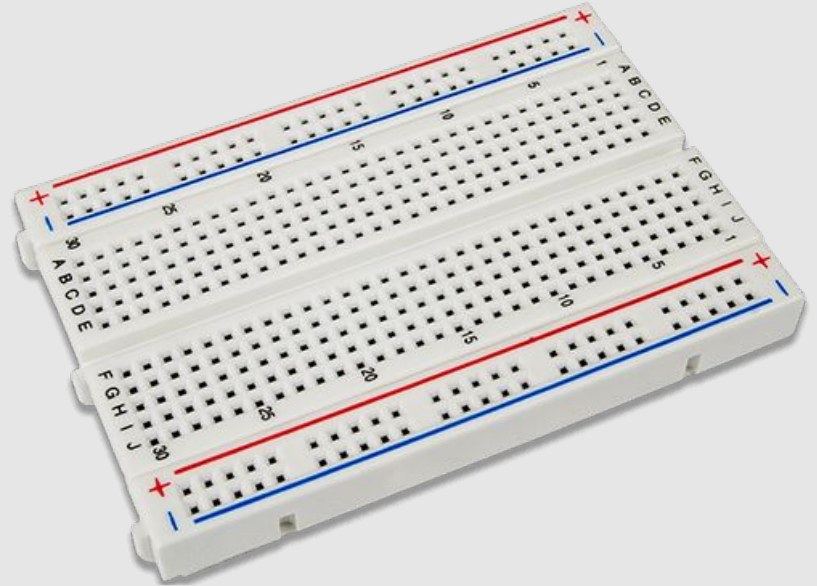- Used to make temporary connections to test circuits
- Rows are connected together with a jump in the middle
- Column bars used for power and voltage levels




Breadboard Connections

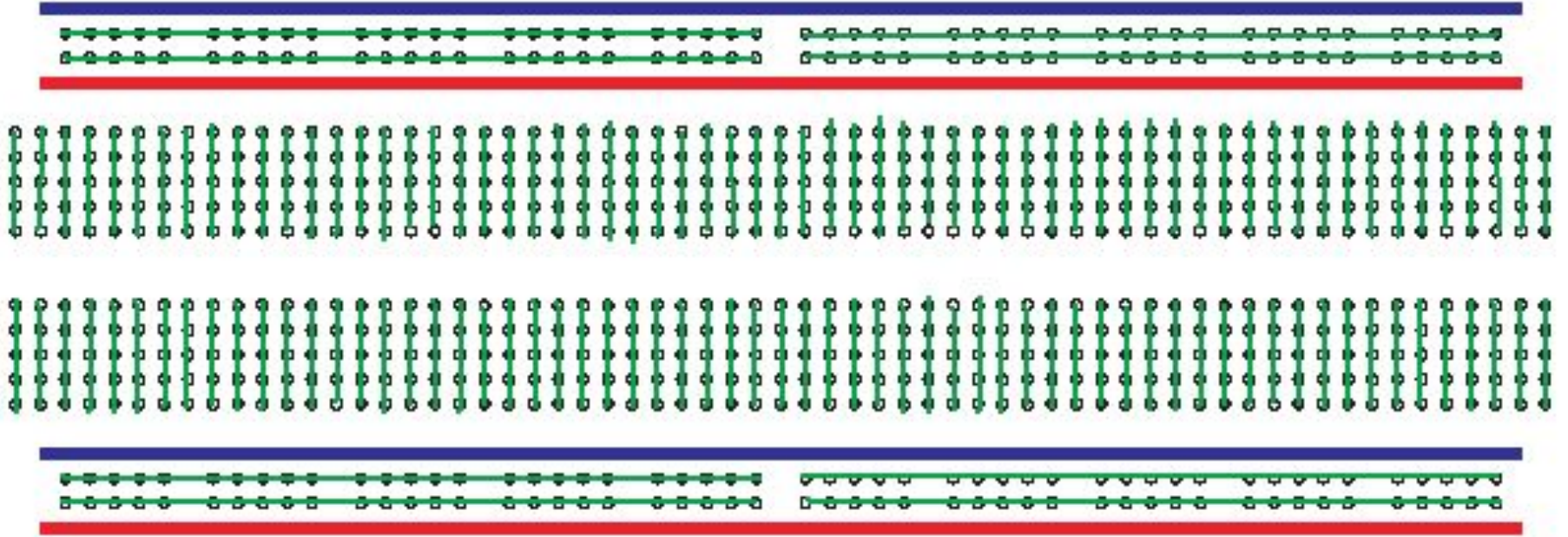

LED Circuit

- Construct this circuit
- Power supply will be 9V
- Calculate Resistance needed
- LED needs 20mA and 2V

$$V = I \times R$$

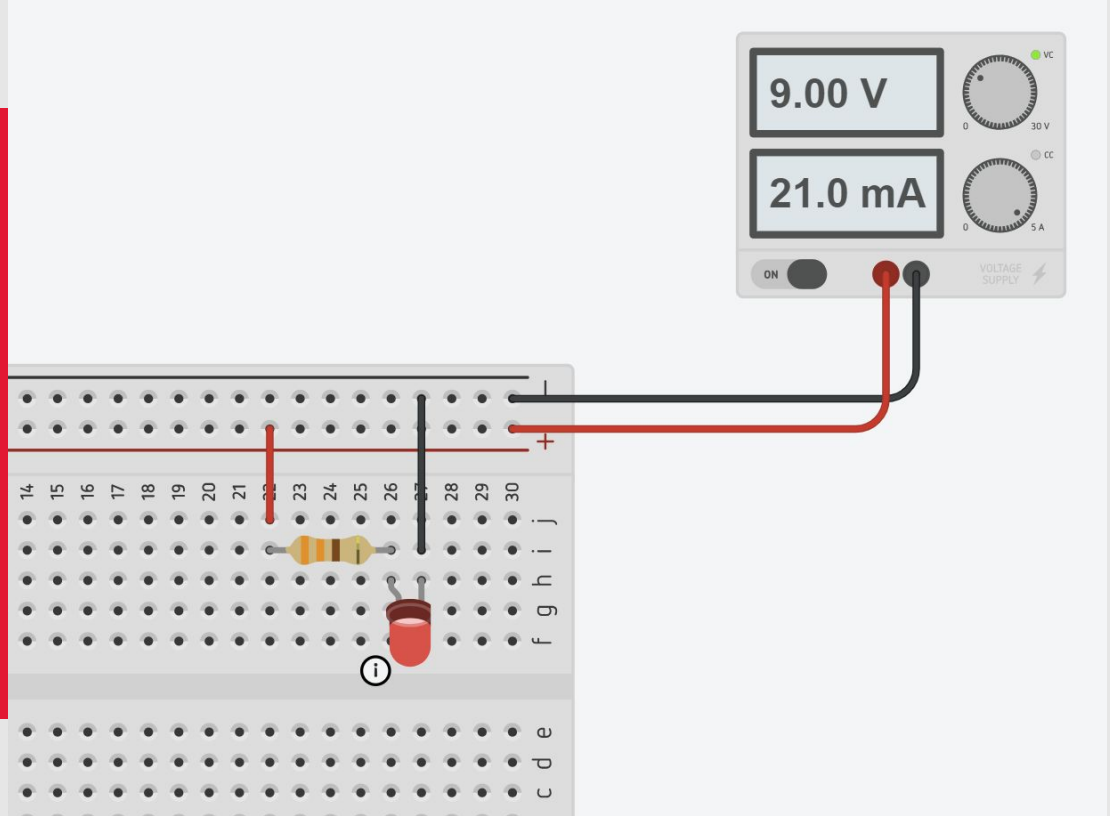



Part 3



Controlling Circuits

Transistor

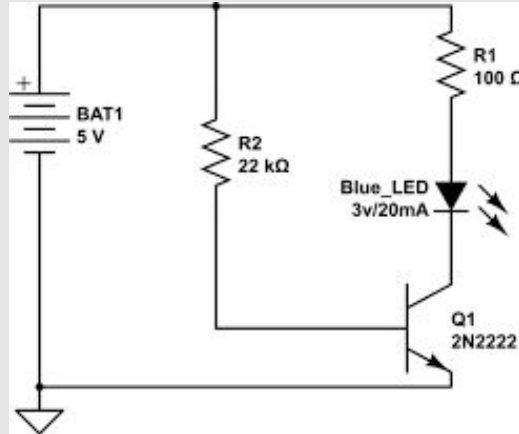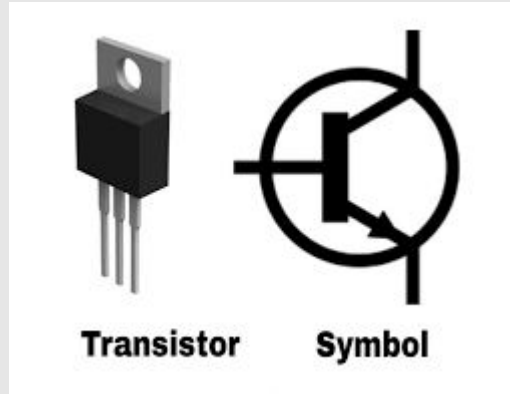
- Electrical Switch
- One terminal impacts current flow between the other two terminals



MOSFET vs. BJT


MOSFET

- Voltage Dependent
- Gate control pin

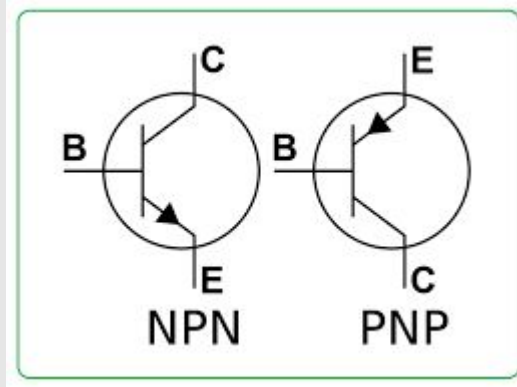

BJT

- Current Dependent
- Base control pin

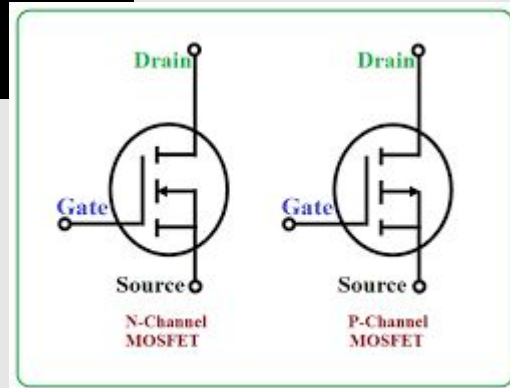

Buttons

- Temporary electrical connection
- Connection formed when pressed
- Physical Switch




Pole and Throw

Pole

- Number of switches


Throw

- Number of connections

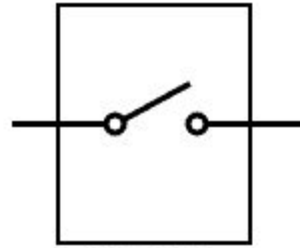


SPST

Single Pole Single throw

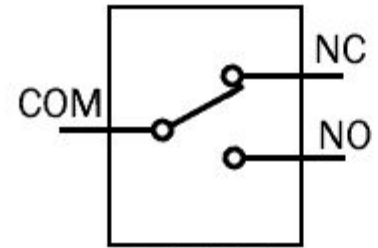


SPDT

Single Pole Double Throw

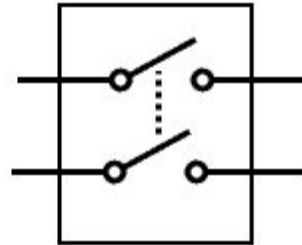

DPST

Double Pole Single Throw

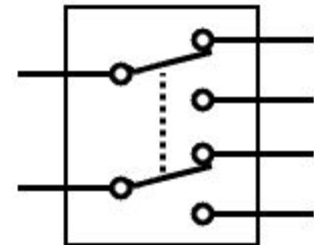

DPDT

Double Pole Double Throw

Momentary vs Latching

Momentary Switch

- The state of the switch is **directly set** by depression (pressed = on, idle = off)



Latching Switch


- A state transition is **initiated** by depression (it remembers)



Example Project

Is this too much? Idrk

It showcases
momentary
pushbuttons and the
switching functionality
of transistors which I
think we need to do if
we mention both

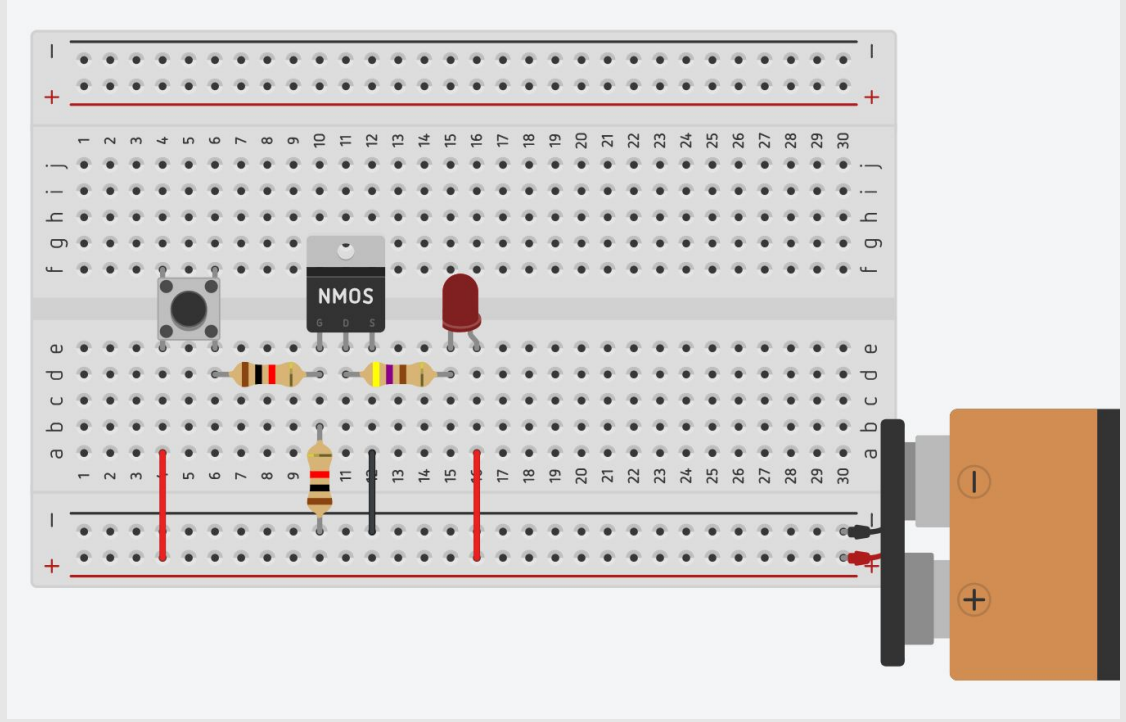

Part 4



Measuring Circuits

Multimeter

- Measures many different quantities
- DC and AC voltage, current, resistance, frequency, capacitance, inductance, etc
- Measurements are done with two probes



Probes


- Wires that **connect measurement tool** to circuit
- Red goes to positive side of measurement
- Black goes to negative side of measurement



Measuring Voltage

- Voltage is measured between two points on the circuit
- Make sure red probe is on the voltage side
- Set multimeter to measure voltage
- Place probes at the two locations to measure across

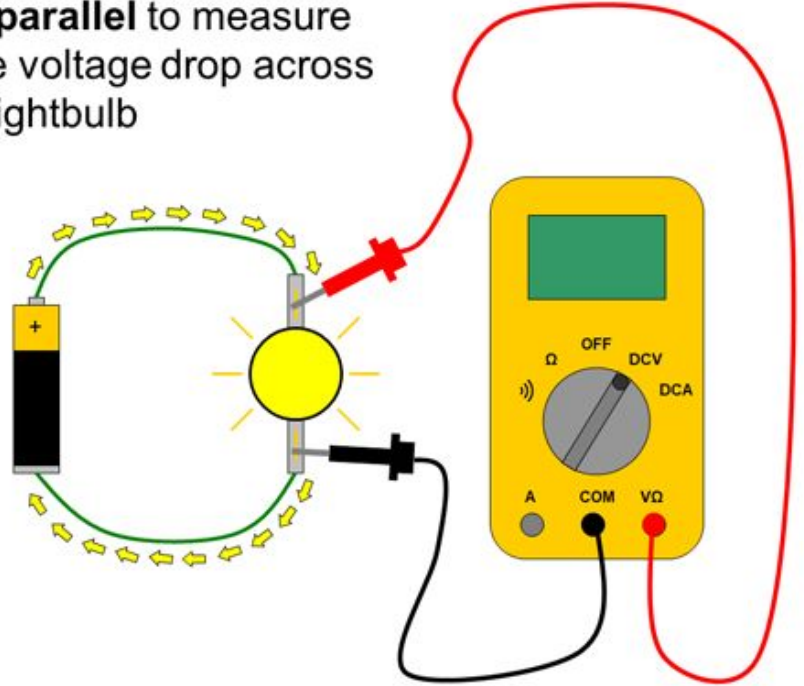
Connect a multimeter in **parallel** to measure the voltage drop across a lightbulb



<https://www.sciencebuddies.org/science-fair-projects/references/how-to-use-a-multimeter>


Practice Measuring Voltage

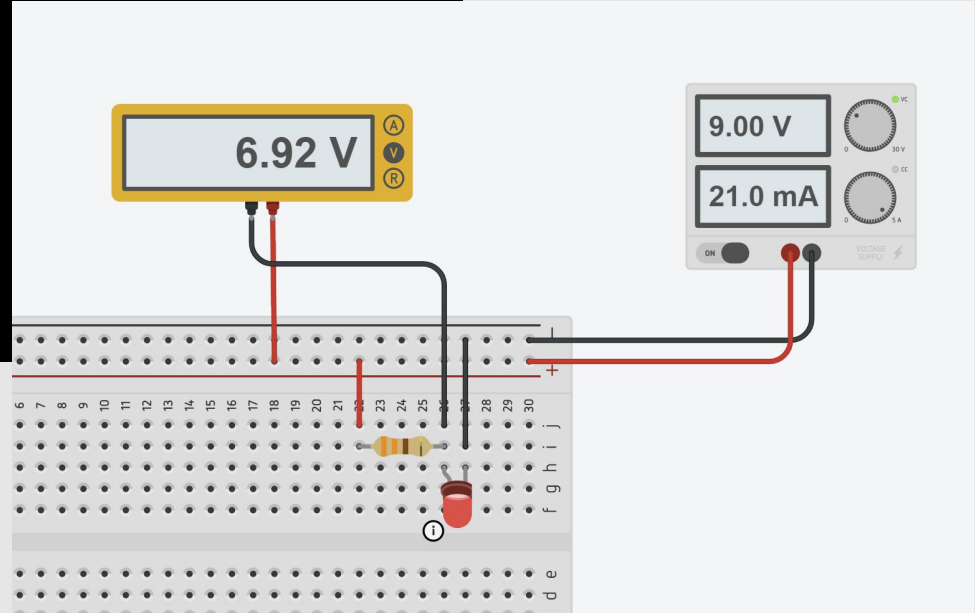- Turn on the power supply
- Measure the voltages across the resistor and LED



Measuring Other Values

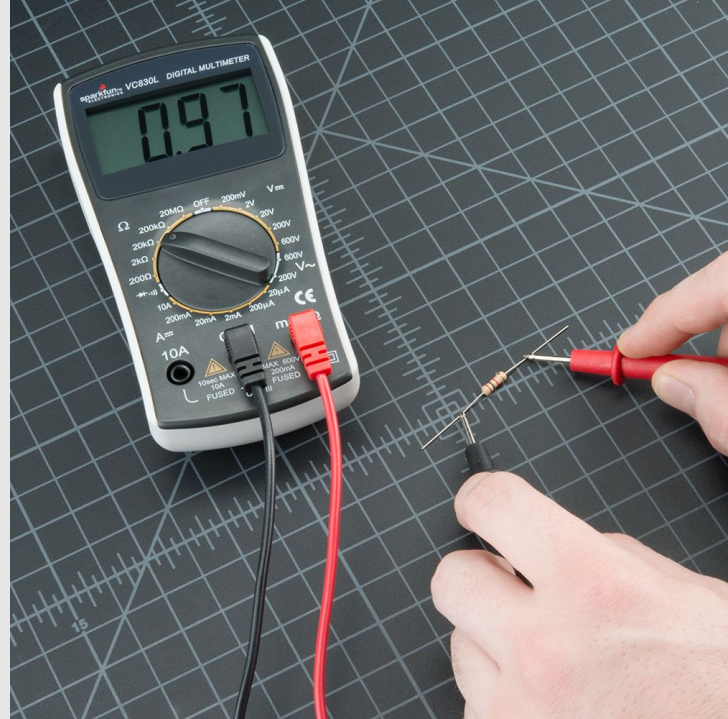
- Resistance, frequencies, capacitance, continuity, etc
- Measured using the same port as voltage
- Except for frequency your circuit should be off for these measurements



<https://learn.sparkfun.com/tutorials/how-to-use-a-multimeter/measuring-resistance>


Practice Measuring Resistance

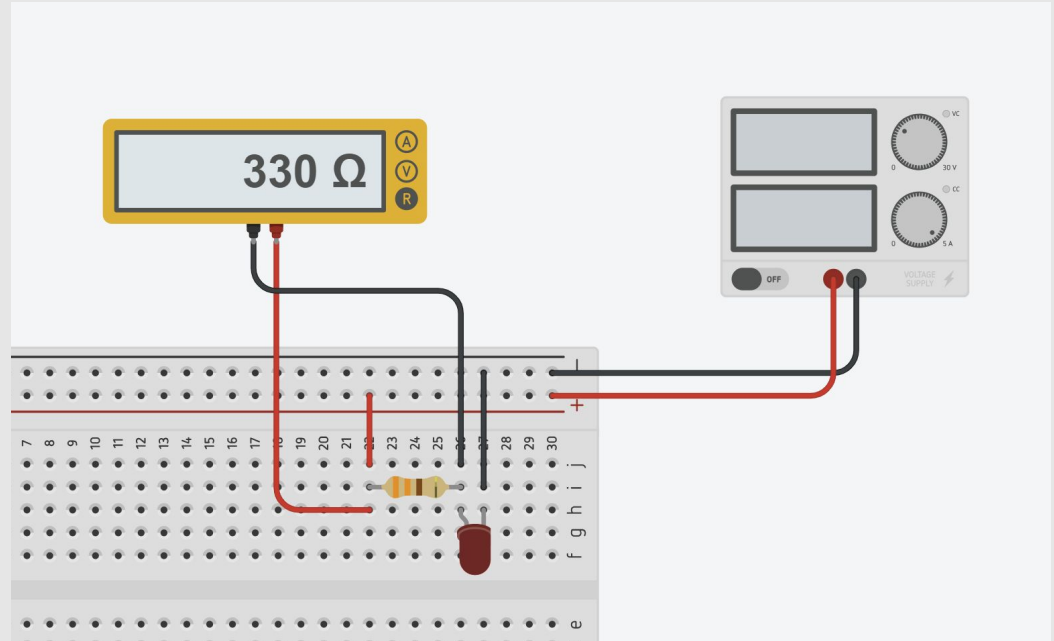- Turn off power supply
- Measure the actual resistance of the resistor
- Using your previous voltage measurement calculate the current




Measuring Current

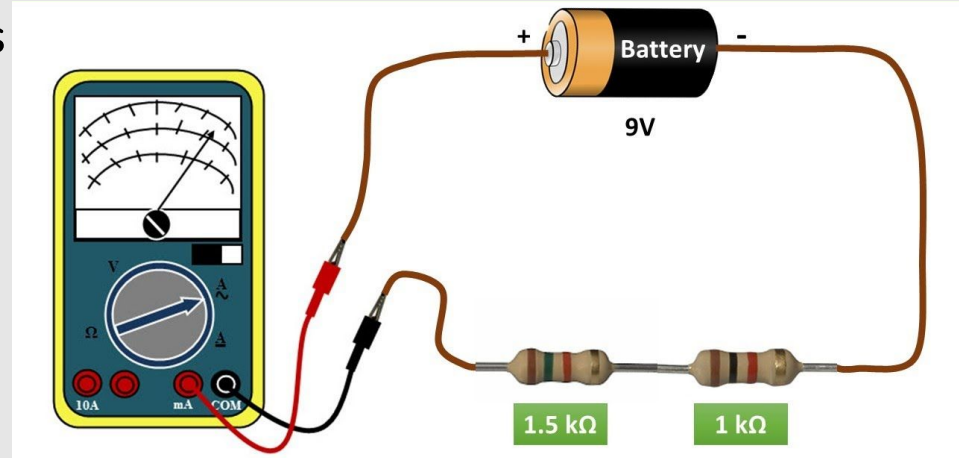- Current is measured differently than voltage
- Need to break open the circuit and measure between the points you broke open
- This is a **single-point** measurement
- Use the current port instead of the voltage port



Practice Measuring Current

- Rearrange circuit to measure current
- Turn power supply back on
- Measure current
- Use measured current and voltage measurements to determine power

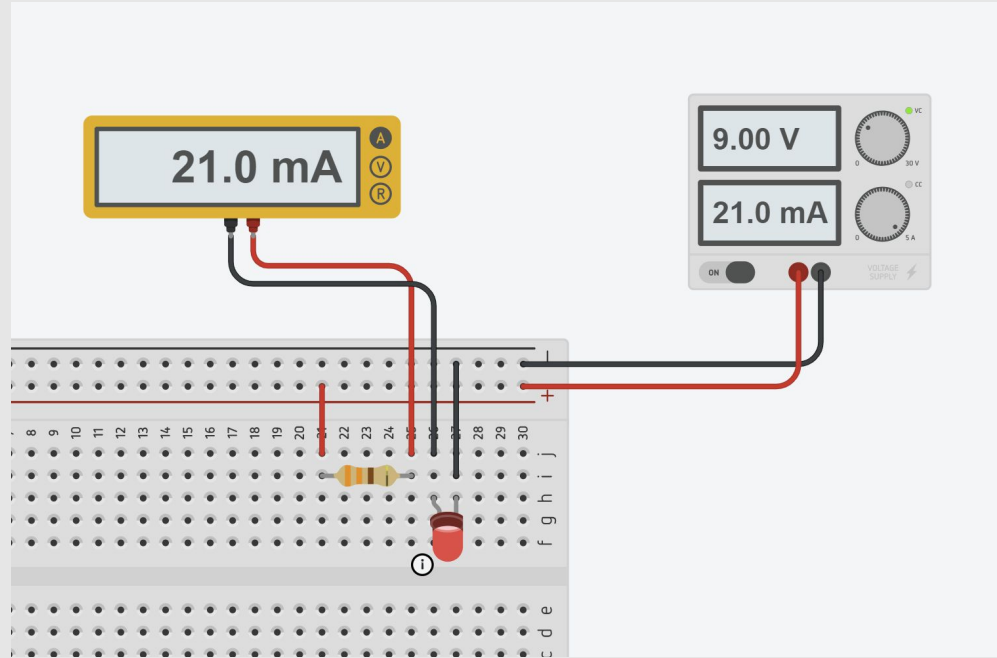



Part 5



Building Circuits

Types of connections

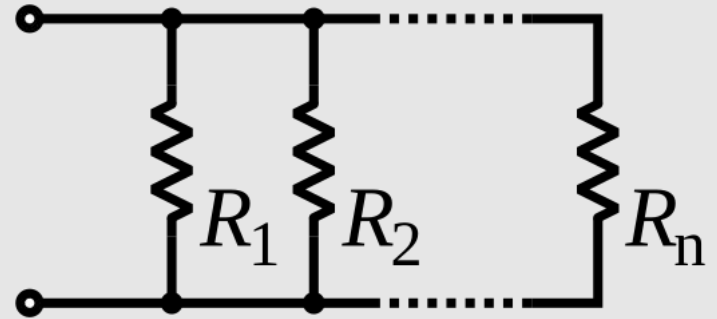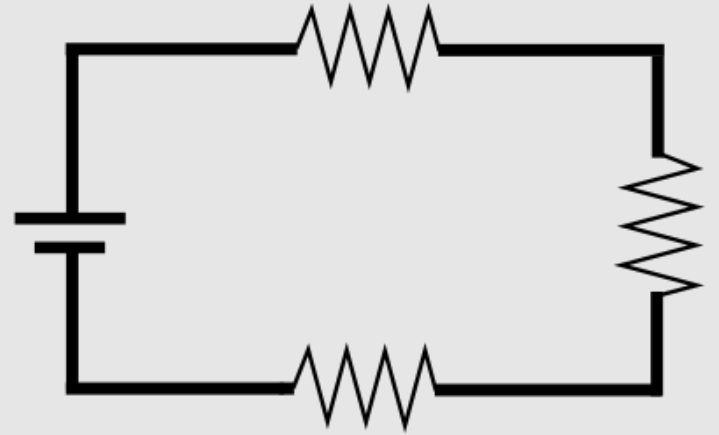- It is possible to connect the same set of components in different ways.
- The different orientations drastically affect the electrical performance.




Series connection - Theory

- Singular path for current
- Current is **constant** through all components
- Voltage is used up **crossing** each component.
- Voltage is **summed** across the connection.

$$V_t = V_1 + V_2 + V_3$$

$$I_t = I_1 = I_2 = I_3$$

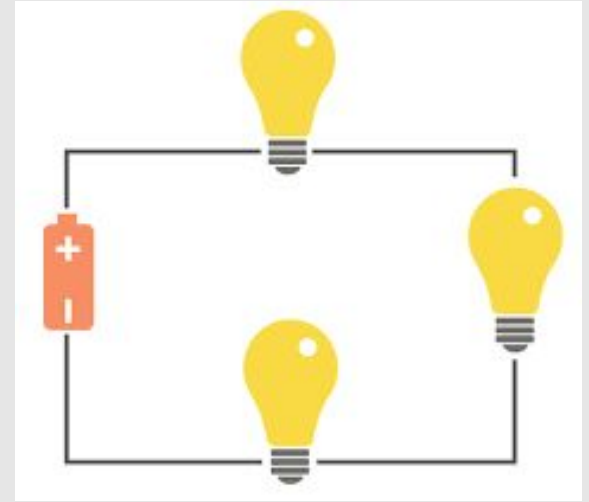


Parallel connection - Theory

- Multiple paths for current
- Current is **divided** among each branch.
- Each component is place **across** voltage source
- Voltage is the **same** across all components.


$$V_t = V_1 = V_2 = V_3$$

$$I_t = I_1 + I_2 + I_3$$

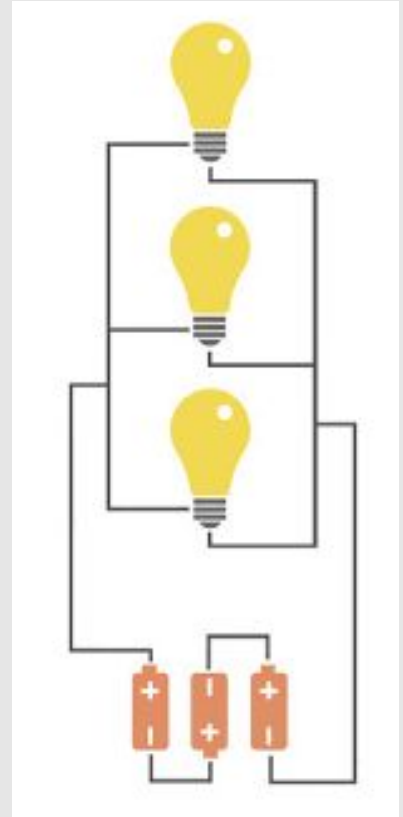


Series connection - Practice

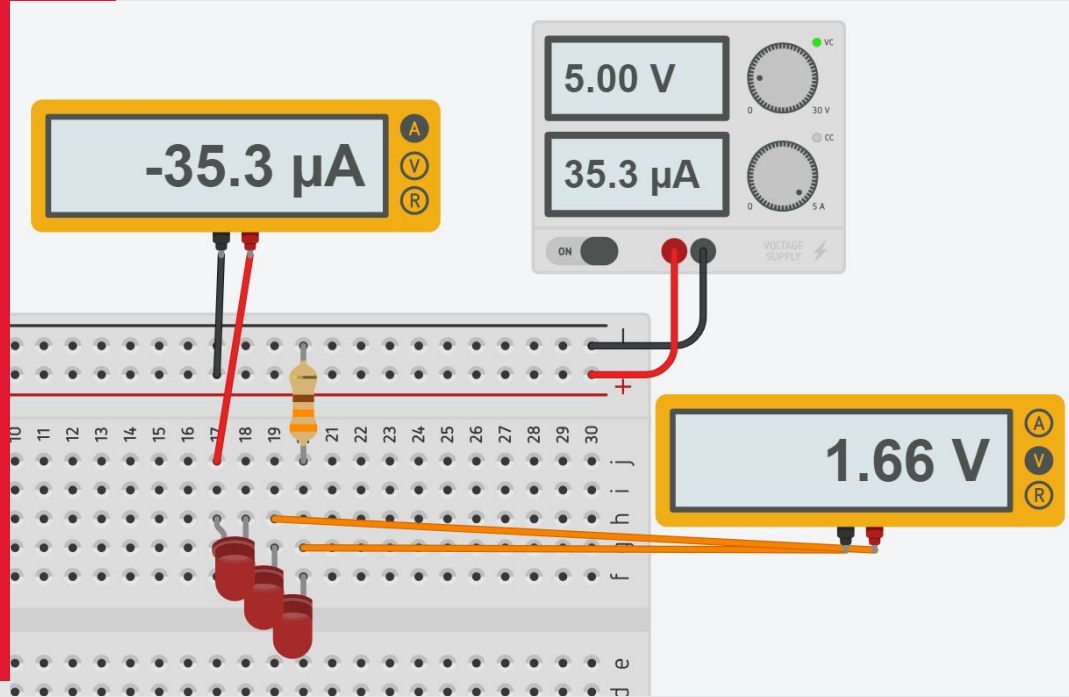- Note how each LED has **voltage drop** across it and how this affects brightness.
- Note how current is the **same** at all parts of the circuit
- Experiment! See how adding or removing LED's changes voltage.





Parallel connection - Practice

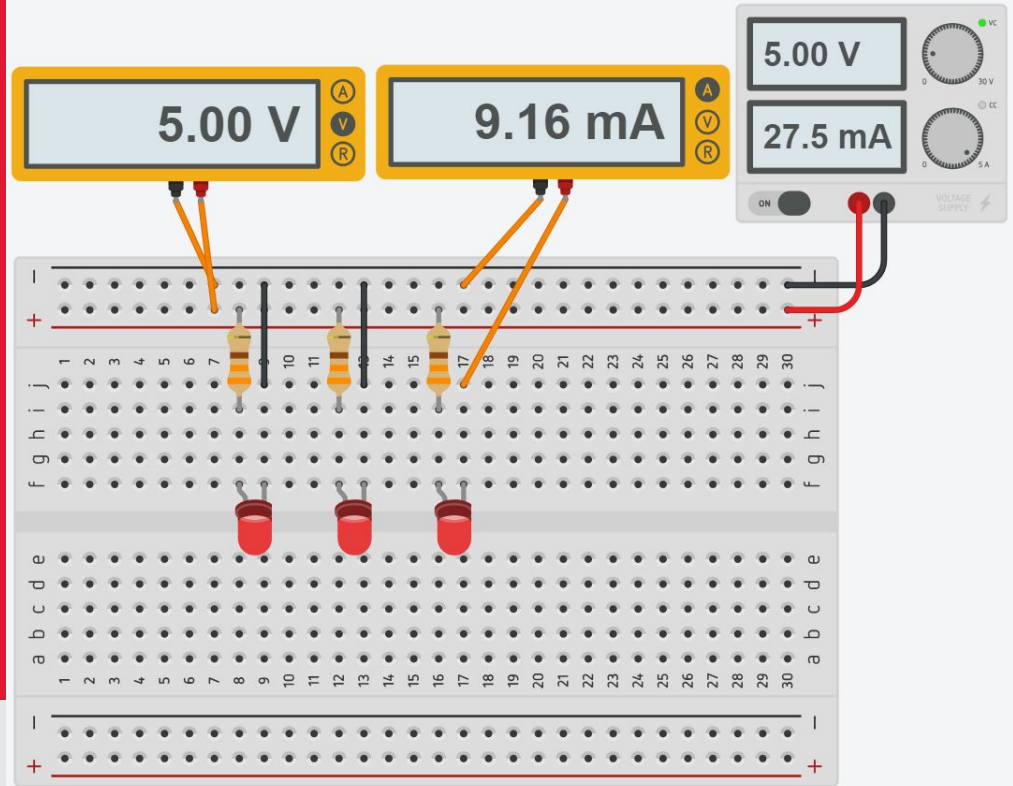- Since each branch has the same resistance current in each branch is identical.
- Voltage across each branch is **identical**.
- Experiment! See how changing resistances changes currents.



Next Workshop

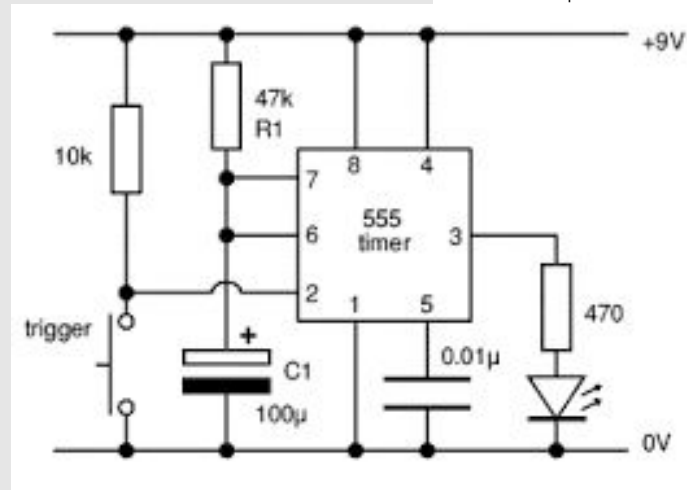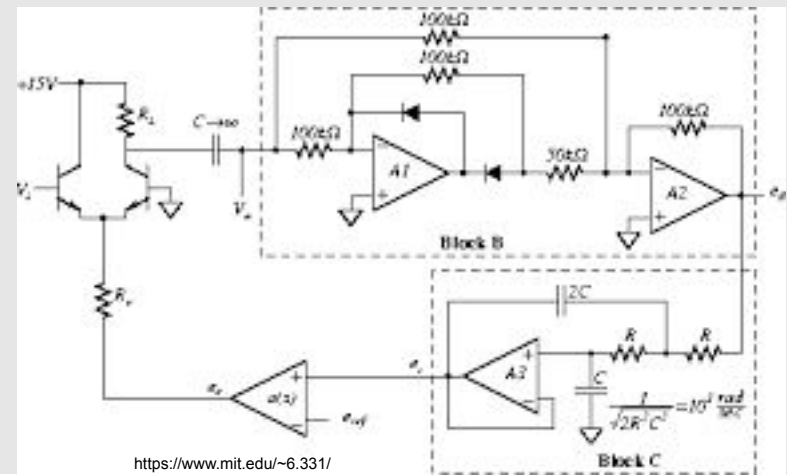- What is a circuit
- Parts of a circuit
- Basic circuit elements



Come visit the IES!



1115 AJC
Open Lab 2:00- 7:00 PM Weekdays



Thank you!

Please give us your feedback!

<https://tinyurl.com/6eayw8r8>